

(4)

Unit-III / FkâF-III

7½

A

(Printed Pages 4)

6. Write short notes on the following :

- (i) Step up chopper operation
(ii) Step down chopper operation

efcve hej mehle veeš edekles :

- (i) medejce Deje ekeā keā GÜüeve ðeueueve
(ii) medejce Deje ekeā keā Dejeceve ðeueueve

7. What is a saturable reactor ? How it can be converted into magnetic amplifier ? Give the circuit of a magnetic amplifier and explain its working.

medeue ej Uekesj kelee netee nw? Fmes Ügeyekaele ðejeoleka cellkame
yeoue mekealeas nP Skeā Ügeyekaele ðejeoleka keā j heL Kehdele
Deej Fmekaeā keaele& edeDe mecePeefUes

Unit-IV / FkâF-IV

7½

8. Draw circuits for single phase half bridge and full bridge invertor circuit. Compare the performance of both the circuits.

Skeā keauē DeaeñegDeej heCemedegDevlejel eekae heej heL Kehdele
oerelhef hel eelkai keaele& keā legevee keaepefUes

9. Discuss the workign of ac static switch in detail. How devices are protected in power electronics?

AC emLej emJeñekaeā keaeleDe ellmleej mes mecePeefUes heej
Fukas arkena cellf JeeFmene keae kames mej effele ekauee paelle n?

Roll No. _____

S-615

B.Sc.(Part-II) Examination, 2015

ELECTRONICS

Paper - III

(Industrial & Power Electronics)

Time Allowed : Three Hours] [Maximum Marks : 50

Note : Answer five questions in all. Question No.

1 is compulsory. Attempt one question from each unit.

kegue heeße ðellveelkai Göej oepes~ ðellve meb 1 Deefjeeljew
ðelUekai FkâF mes Skeā ðellve keaepeS~

1. Write short answer of the following :

efcve keā mehle Göej edekles : $2 \times 10 = 20$

- (i) What do you understand by controlled rectifier?

efjeefSele j kešeheleJeme& mes Dehe kelee meceP nP

- (ii) Draw V-I characteristic curve of Thyristor.

LeeFef mšj keā V-I Dejeuee#eCekai Jeaā Kehdele

(2)

(iii) What is a Diac?

[elkaa keelee nee nw?]

(iv) What is a snubber circuit?

mveyej heej hee keelee nee nw

(v) What do you understand by constant frequency chopper operation?

meelje ecer Deej eekaa kei eveljele Deejeele Deejeele mes Deeh
keelee mecePees nP

(vi) Name few solid state devices.

kejU "ame DejemLee ejJeefame kei veece yeleejell

(vii) What are the advantages of static switches over mechanical?

efLej efJeelkai Ueef/Skeka efJeelkai Dehe#ee keelee heaeJe:
nP

(viii) Define 'Quiescent Current' of Magnetic Amplifiers.

UegyekaaDejeelkaa kea'Meevl e Oej e' keashef Yeekele keepejell

(ix) Name performance parameters of invertors?

DevleJeekaa eheeoove Deelue kei veece eueKeW

(x) What do you understand by pulse width modulation in reference to invertors?

DevleJeekaa mecye0e cellmhab keeueeJeeDe efeJeeCe mes keelee
mecePees nP

(3)

Unit-I / EkeF-I

7 1/2

2. Define various performance parameters of a rectifier. What is the significance of form factor and harmonic factor?

eb° keaj er kei eeljeve eheeoove Deelueeell/keer heej Yeece oepjles
'Deekaa leška' Deej nejceeskeak leškaa keelee olMeetee nw

3. Define "turn on" and "turn off" thyristor. Explain in brief few methods to 'turn on' and 'turn off' Thyristor .

LeeFij mšj kei 'Deej cYe mecele' Deej 'ejeOejeve mecele' keahhef Yeece
oepjles LeeFij mšj keas 'Deej cYe' Deej 'Deekaa' keaj ves kei kegU
lej ekeell/keas me#ehle cellmecePeeFles

Unit-II / EkeF-II

7 1/2

4. Explain the principle of 'on-off' and phase angle control in AC voltage controller. Derive the expression for RMS output voltage and RMS output current.

'AC JeesiŠpe ejeUdekaellcell Ueuet yeb' Deej 'keauue keashe efeJeeCe'
kei efeEevle keas mecePeeFles RMS efeieje JeesiŠpe Deej RMS
efeieje kei JUdekaa keaCevee keasheFles

5. Explain the working of a single phase full converter with RL load.

RL Yej JeueSkeak keauue heCelleJeeDea keaSeJee keasmecePeeFles