

Commutation Techniques of Thyristors.

- Commutation is defined as the process of turning-off a thyristor.
- Turn-off of a thyristor means, bringing the device from forward-conduction mode to forward-blocking mode.
- Turn-off process of thyristor requires
 - ↳ (a) Anode current to be reduced below holding current
 - ↳ (b) application of a reverse voltage to remove the extra charge carriers and regain its blocking state.

Classification of commutation techniques.

- Commutation techniques of thyristors are classified, based on
 - ↳ the manner in which anode current is reduced to zero. and,
 - ↳ the configuration of the commutating circuits.

- One method of classification is as follows.

① Natural Commutation or line Commutation (class F)

② Load Commutation or Self commutation (class A)

③ Forced Commutation.


↳ (a) Resonant - Pulse Commutation (class B)

↳ (b) Complementary Commutation (class C)

↳ (c) Impulse commutation (class D)

① Natural Commutation or Line Commutation (Class F)

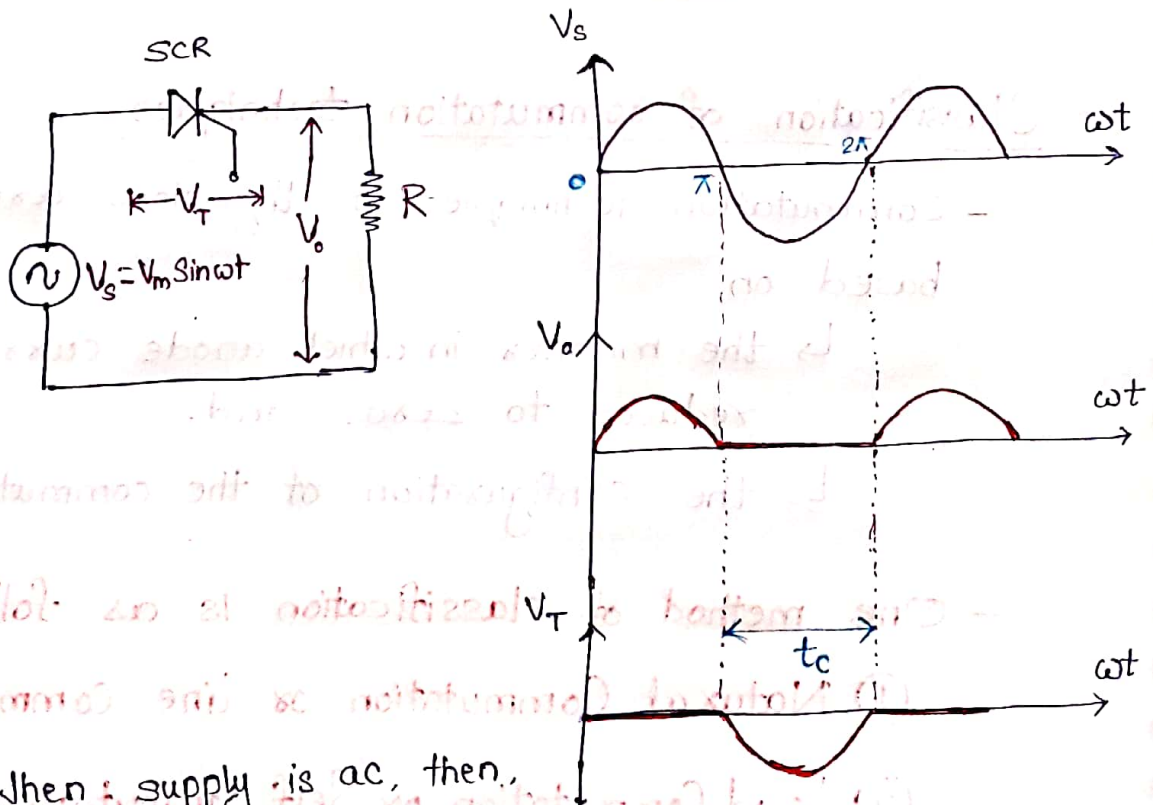- Natural commutation of thyristor occurs only when the supply is ac. Nature of supply automatically takes care of commutation. So, it is known as natural commutation or line commutation.



- When supply is ac, then, the anode current through the thyristor automatically pass through zero at the end of every positive half cycle i.e. at $\omega t = \pi$.

- So, anode current becomes zero after positive half cycle.
- The supply voltage also applies a reverse bias voltage across the SCR in the negative half cycle. This reverse bias ensures that SCR regains its blocking capability.

Applications:

- Phase-controlled converters,
- line-commutated inverters,
- ac-voltage controllers,
- step-down cyclo-converters.


② Load Commutation or Self commutation (class A).

- Load commutation or class-A commutation is possible in thyristor circuits supplied from dc source. It is not possible in ac circuits.

- For load commutation to occur, the nature of load circuit should be such that, when it is energized from a dc source, the current has a tendency to decay to zero value, due to load.





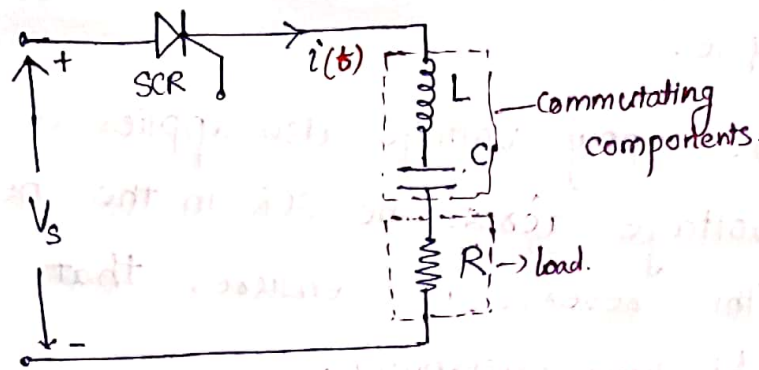It is possible when load contains R, L and C parameters and satisfy underdamped condition.



- When the circuit is energised from dc source, the current first rises to maximum value and then decays to zero. So, thyristor gets turned-off. Voltage of capacitor applies a reverse bias across the thyristor after turn-off.
- Load commutation is also known as resonant commutation or self-commutation.
- Application :- Series inverter circuit.

Waveforms :-

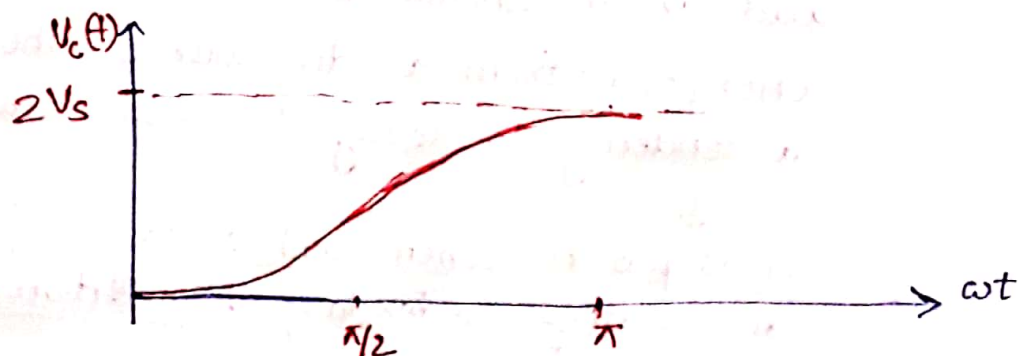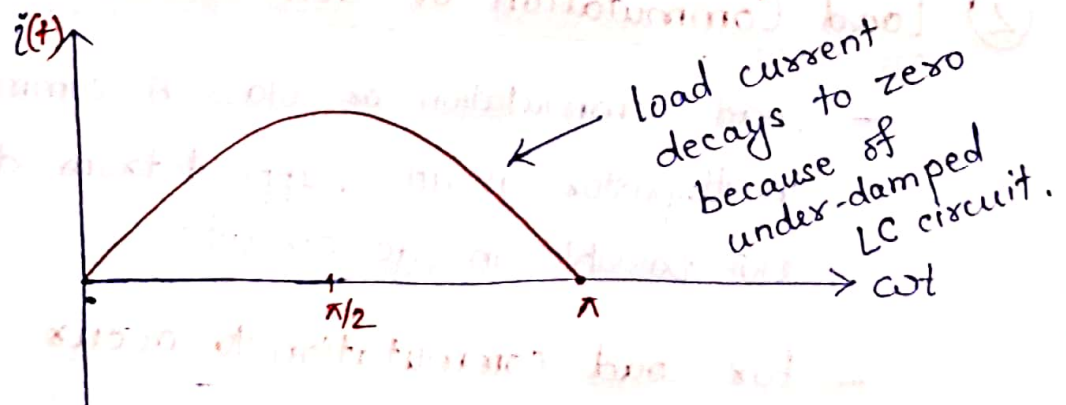

- Load current is like charging current of capacitor.
So, initially after turning on of thyristor, current $i(t)$ increases, then it reaches maximum value and then decays to zero.

- At $\omega t = \pi$, when thyristor current decays to zero, the voltage stored in capacitor is $2V_s$.

So, at $\omega t = \pi$, voltage across thyristor is,

$$V_T = -2V_s + V_s = -V_s$$

↓
So, ~~ca~~ net reverse voltage appears across the thyristor when current decays to zero.

→ Conduction angle of thyristor, $\omega t_0 = \pi$.

→ Conduction time of thyristor, $t_0 = \frac{\pi}{\omega}$

Here, ω_0 is known as resonant frequency of the LC circuit.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

→ $\therefore$ Conduction time, $t_0 = \frac{\pi}{\omega_0} = \pi \sqrt{LC}$

→ For satisfying the condition of under-damping,

$$\frac{R}{2} < \sqrt{\frac{L}{C}}$$

$$\text{or } R^2 < \frac{4L}{C}$$