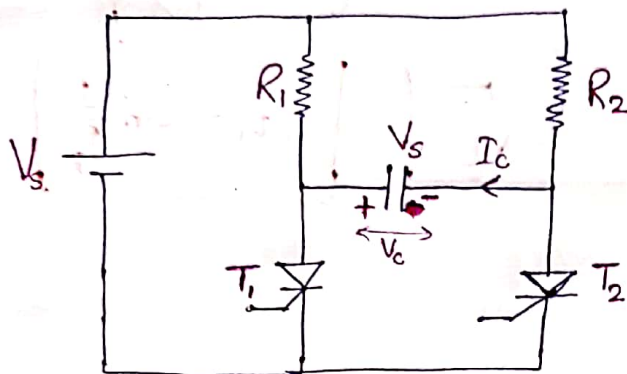


⑥ Complementary Commutation or Class C commutation.



Complementary Commutation

- In this technique two thyristors are used for carrying the load current alternately.
- One thyristor is turned-off by turning on the other thyristor. The load current also transfers from the outgoing thyristor to incoming thyristor.
- In this, one thyristor takes care of the commutation of the other and vice-versa. So, it is also known as complementary commutation.

Assumption :-


- 1) Capacitor C , is charged initially to voltage V_s , with the polarity marked above in circuit diagram.
- The operation of the commutation circuit can be understood in two steps.

Step 1 :-

At $t = 0 \text{ sec}$.

T_1 is turned ON.

T_2 is off.

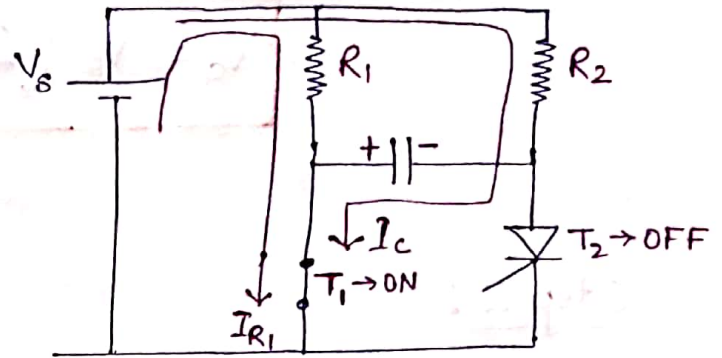

- The moment T_1 is turned ON, immediately T_2 becomes OFF, due to reverse voltage applied by capacitor C.

- So, when thyristor T_1 is turned ON, current flows ~~in~~ through it in the manner shown above.

- The thyristor current I_{T_1} has two components.


$$I_{T_1} = I_{R_1} + I_C$$

- We know,

$$I_{R_1} = \frac{V_s}{R_1}$$

$$\text{and, } I_C = \frac{(V_s + V_s)}{R_2} e^{-t/R_2 C}$$
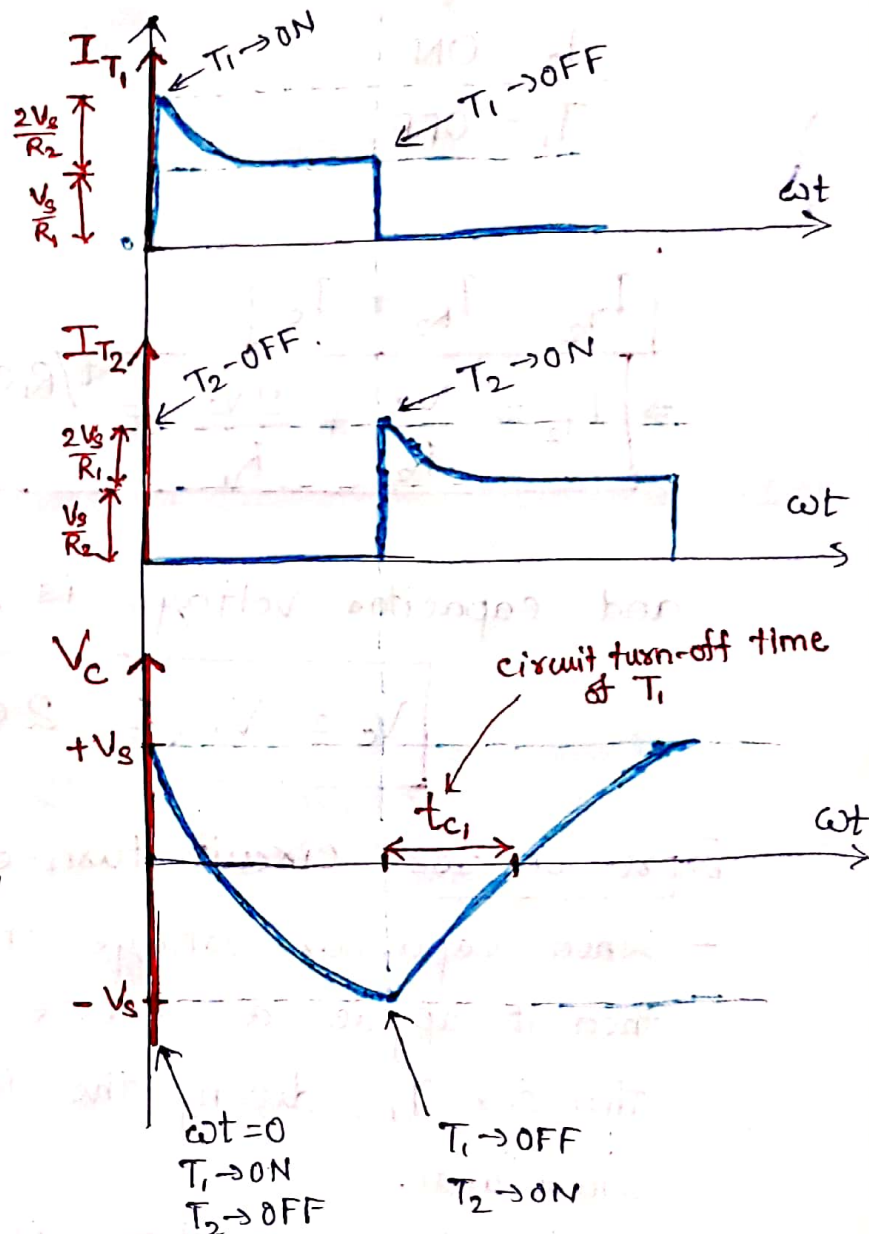
$$\text{So, } I_{T_1} = \frac{V_s}{R_1} + \frac{2V_s}{R_2} e^{-t/R_2 C}$$



- Capacitor voltage is given by.


$$V_c = V_s (2e^{-t/R_2 C} - 1)$$

Step 2 :-

At $t = t_1$

$T_2 = \text{ON}$

$T_1 = \text{OFF}$

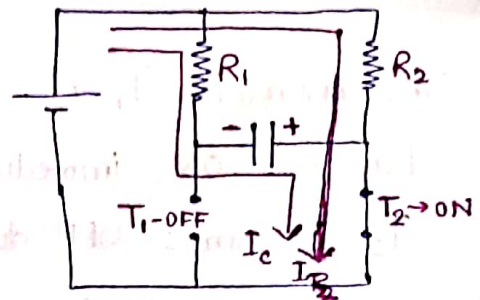

$$I_{T_2} = I_{R_2} + I_c$$

$$\Rightarrow I_{T_2} = \frac{V_s}{R_2} + \frac{2V_s}{R_1} e^{-t/R_1 C}$$

and capacitor voltage is given by.

$$V_c = V_s (1 - 2e^{-t/R_1 C})$$

Expression for circuit turn-off time

- When capacitor voltage changes from $-V_s$ to $+V_s$, then it applies a reverse bias voltage across thyristor T_1 , during the interval t_{c1} , shown in waveform.
- Circuit - turn-off time is the duration for which reverse bias voltage is applied across the thyristor, to enable it to regain its blocking capability.

- So, putting time as t_{c1} in the voltage expression for capacitor in step 2 and equating it to zero, we can find the value of t_{c1} .
- We equate the capacitor voltage to zero, as, at t_{c1} , $V_c = 0$, from the waveform above.

$$\therefore V_c = V_s (1 - 2e^{-t_{c1}/R_1 C}) = 0$$

$$\Rightarrow 1 - 2e^{-t_{c1}/R_1 C} = 0$$

$$\Rightarrow e^{-t_{c1}/R_1 C} = \frac{1}{2}$$

$$\Rightarrow \frac{-t_{c1}}{R_1 C} = \ln\left(\frac{1}{2}\right)$$

$$\Rightarrow \boxed{t_{c1} = R_1 C \ln(2)}$$

Imp

- So, circuit turn-off time for thyristor T_1 is $t_{c1} = R_1 C \ln(2)$.
- Similarly, circuit turn off time of $T_2 = t_{c2} = R_2 C \ln(2)$
- Peak value of current through T_1 , $I_{T_1} = V_s \left[\frac{1}{R_1} + \frac{2}{R_2} \right]$
- Peak value of current through T_2 , $I_{T_2} = V_s \left[\frac{2}{R_1} + \frac{1}{R_2} \right]$