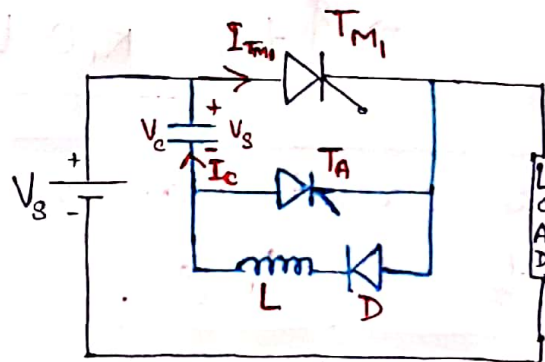


© Voltage Commutation or Impulse Commutation or Class D commutation.

- In this method of commutation, a reverse voltage is suddenly applied across the thyristor, to turn it off. So, it is also known as Voltage commutation.



- This type of commutation is also known as auxiliary commutation, as an auxiliary thyristor T_A is used to turn-off the main thyristor T_M .

Assumptions:-

- 1). Capacitor is initially charged with V_s volts, and polarity is as marked in the circuit diagram.
- 2) Load current is assumed to be constant.
- 3) Before $t=0$ sec., both T_M and T_A are off.


- Operation of the commutation circuit can be understood in two steps.

Step 1 :-

at $t=0$ sec.

$T_M \rightarrow$ turned ON.

$V_c = +V_s$

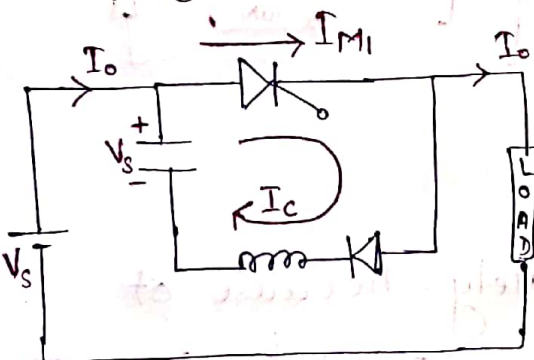

$$I_{M1} = I_o + I_c$$

and

$$I_c = I_p \sin \omega_0 t$$


$$\Rightarrow I_c = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t$$

At end of step 1.

$$\rightarrow V_c = -V_s$$


$$\rightarrow I_c = 0$$

$$\rightarrow I_M = I_o$$

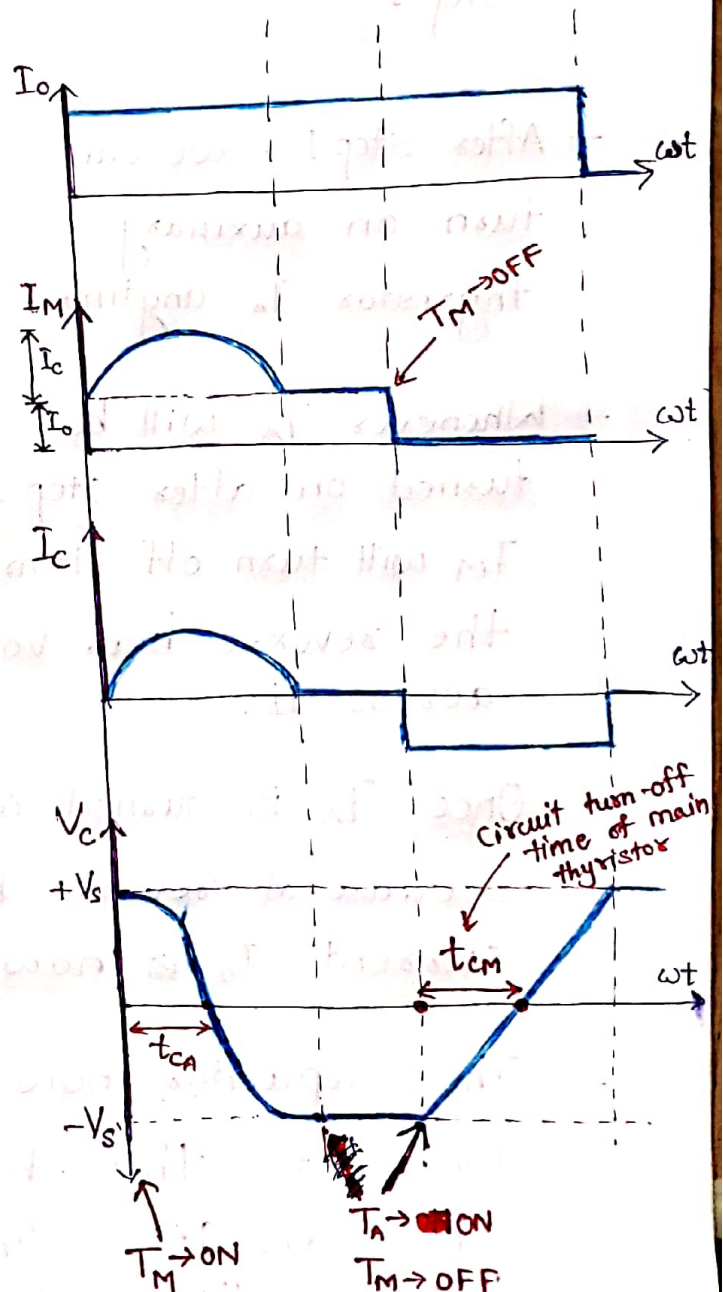


Step 2 :-

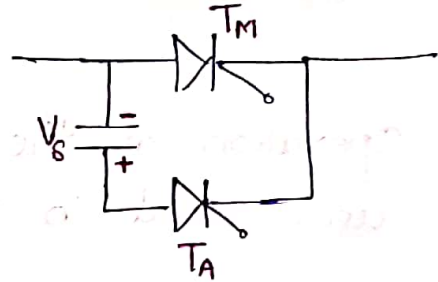- The capacitor voltage changes or reverses its polarity at the end of step 1.



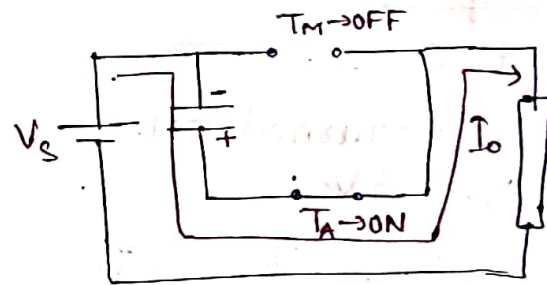- After step 1, we can turn on auxiliary thyristor T_A anytime.



- Whenever T_A will be turned-on after step 1, T_M will turn-off immediately, because of the reverse bias voltage applied by capacitor across it.
- Once T_A is turned ON, T_M is turned-off because of reverse bias voltage and load current, I_o now flows through T_A .
- The capacitor now charges from $-V_s$ to $+V_s$, but this charging is linear and not sinusoidal. It is linear because load current I_o , passing through it is maintained constant by load.

Finding circuit-turn-off time

→ For main thyristor, circuit-turn-off time, t_{cm} can be obtained from the capacitor voltage expression. We know.

$$V_c = \frac{1}{C} \int I_c dt.$$

Now, we know $I_c = I_o$ and time is t_{cm} . and $V_c = V_s$.

$$\Rightarrow V_s = \frac{I_o}{C} \cdot t_{cm}$$

$$\Rightarrow t_{cm} = \frac{V_s \cdot C}{I_o}$$

→ For Auxiliary thyristor, when T_M is ON, reverse voltage is applied for ~~the~~ half cycle of discharging period. i.e. for $\omega t = \frac{\pi}{2}$.

$$\omega_0 t_{CA} = \frac{\pi}{2}$$

$$\Rightarrow t_{CA} = \frac{\pi}{2} \times \frac{1}{\omega_0}$$

$$\Rightarrow t_{CA} = \frac{\pi}{2} \sqrt{LC}$$

$$\left(\because \omega = \frac{1}{\sqrt{LC}} \right)$$

→ Circuit turn-off time of $T_M = t_{cm} = C \frac{V_s}{I_o}$

→ Circuit turn-off time of $T_A = t_{CA} = \frac{\pi}{2} \sqrt{LC}$

- Peak value of current through $T_M = I_o + V_s \sqrt{\frac{C}{L}}$ and through $T_A = I_o$

- Minimum time required to turn off T_M after getting turned on at $t=0$ is $\pi \sqrt{LC}$