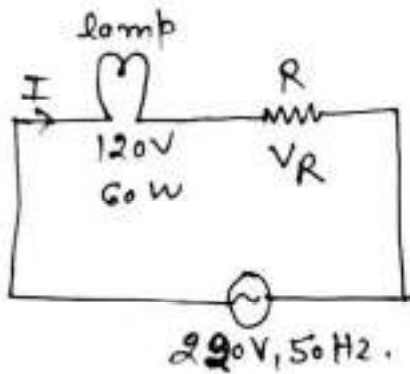


Q.71) A, 60W, 120V lamp Connected across 220V, 50Hz.

A.C. Supply find the Value of (i) Resistor (ii) Inductor Connected in Series with the lamp so that lamp runs on correct Voltage.

Ans. > (i)




"lamp to be considered as pure Resistor"

$$V_R + 120 = 220$$

$$V_R = 100 \text{ V}$$

$$IR = 100 \text{ V}$$

$$R = 200 \Omega \text{ Ans}$$

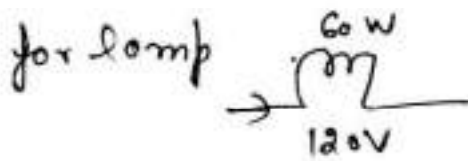


$$P = VI$$


$$I = 60/120$$

$$= 0.5 \text{ A}$$

(ii) for Inductor →

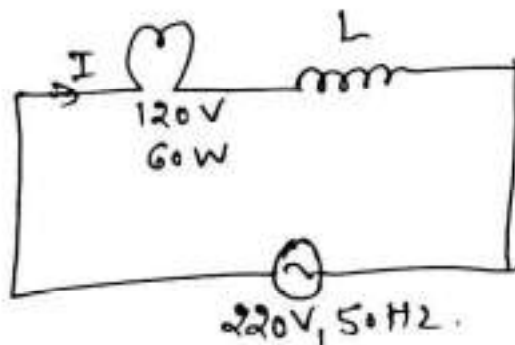

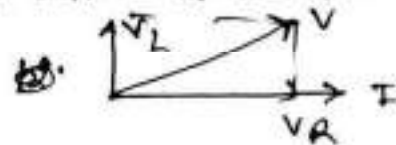"if Inductor is Connected in Series then it behave as like R-L circuit"



$$V_R^2 + V_L^2 = V^2$$

$$(120)^2 + (IX_L)^2 = 220^2$$

$$IX_L = 184.4$$

$$X_L = \frac{184.4}{0.5}$$

$$L = 1.174 \text{ H} \text{ Ans}$$



Ques. 12 > What is Resonance?

Ans. > The Resonance is a phenomenon which takes place in the circuit containing two types of Energy storing element (like Inductor & Capacitor) such that Energy can interchange b/w them.

" At Resonance the Voltage & Current of R-L-C ckt becomes in same phase "

Ques. 13 > Define Resonant frequency and Derive the expression for it. (for Series R-L-C ckt).

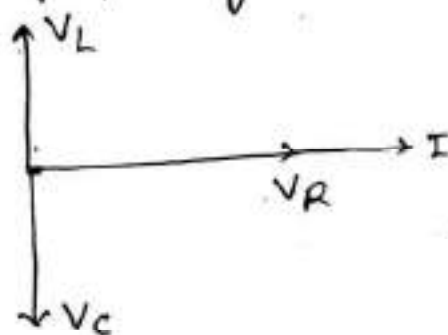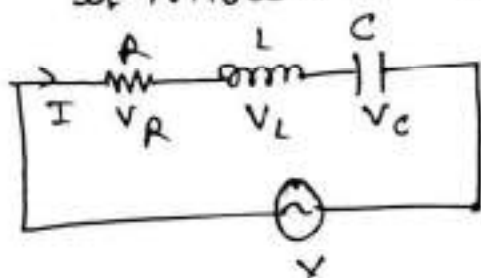Ans. > The frequency at which Resonance takes place is known as Resonant frequency.



Resonance takes place when

$$V_L = V_C$$

$$IX_L = IX_C$$

$$X_L = X_C$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$V_L = IX_L$$


$$V_C = IX_C$$

$$V_R = IR$$

Ques. 14 > What is Resonance curve.


Ans. > The Curve Drawn b/w Current & Frequency for Series R-L-C ckt is known as Resonance curve

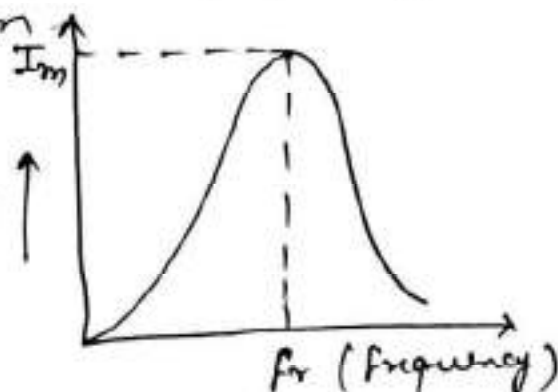f_r → frequency at which Voltage & Current becomes I in same phase.




Ques. 15 > Explain Selectivity & Bandwidth.

Ans. >

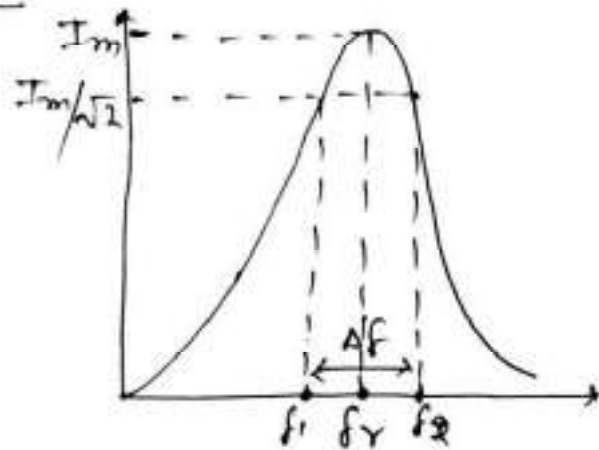

Bandwidth → The band of frequencies either side of Resonance frequency where current becomes $1/\sqrt{2}$ times Maximum current.

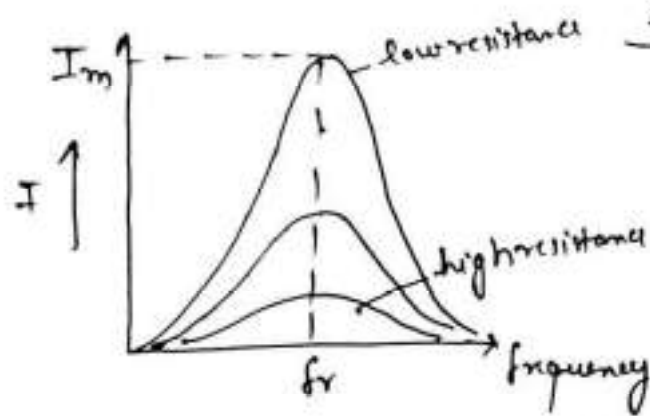
$$\Delta f = f_2 - f_1 \text{ bandwidth}$$



Selectivity → If Resonant curve is highly peaked then it is high selective & if the curve is flat then it is low selective. Selectivity depend upon Resistance of ckt.

Ques. 16 > Derive the Expression for Bandwidth in Series R-L-C ckt >

Ans. >

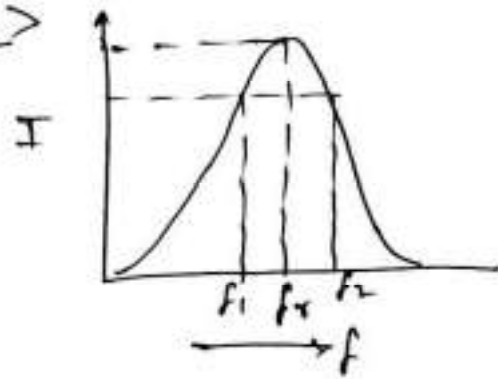

ω_1, ω_2 Corresponding frequencies of point where current is $I_m/\sqrt{2}$

* for maximum current

$$Z = R$$

+ if $I = I_m/\sqrt{2} = \frac{V}{\sqrt{2}R}$
means $Z = \sqrt{2}R$

$$\text{Now } \rightarrow \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{2}R$$

$$X_L - X_C = \pm R$$

⇒ for lower cut off frequency $\omega_1 \rightarrow$

$$\omega_1 L - 1/\omega_1 C = -R$$

$$\omega_1^2 LC - L + R\omega_1 C = 0$$

→ Dividing whole eq. by LC

$$\omega_1^2 + \frac{R}{L} \omega_1 - \frac{1}{LC} = 0$$

now

$$\omega_1 = \frac{-R/L \pm \sqrt{(R/L)^2 + 4/LC}}{2}$$

$$\omega_1 = -R/2L \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{2LC}\right)^2}$$

let $R/2L = \alpha$

$$\omega_r = \frac{1}{\sqrt{LC}}$$

$$\omega_1 = -R/2L \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{\sqrt{LC}}\right)^2}$$

$$\boxed{\omega_1 = -\alpha \pm \sqrt{\alpha^2 + \omega_r^2}}$$

Discarding Negative frequency

$$\omega_1 = -\alpha + \sqrt{\alpha^2 + \omega_r^2}$$

* for upper cutoff frequency $\omega_2 \rightarrow$

$$X_L - X_C = +R$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R$$

$$\boxed{\omega_2 = +\alpha + \sqrt{\alpha^2 + \omega_r^2}}$$

now bandwidth $\omega_2 - \omega_1 = 2\alpha$

$$f_2 - f_1 = \frac{R}{2\pi L}$$

$$\boxed{\Delta f = R/2\pi L}$$

also $\omega_1 \omega_2 = \alpha^2 + \omega_r^2 - \alpha^2$


$$\omega_1 \omega_2 = \omega_r^2$$

$$\omega_1 \omega_2 = \omega_r^2$$

$$\boxed{f_1 f_2 = f_r^2}$$

Ques. 17) Write Down Disadvantages of low power factor How can we improve power factor.

Ans. 7

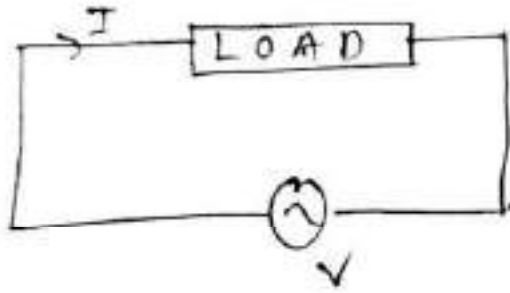





The current for a given load supplied at constant voltage is given by

$$I = \frac{P}{V \cos \phi}$$

∴ If $\cos \phi$ is low then current is high which result following Disadvantages →

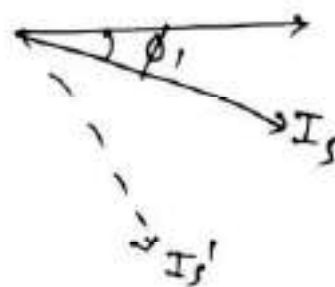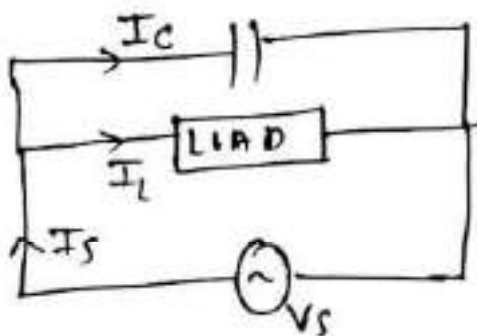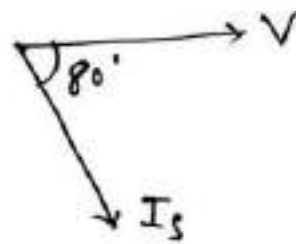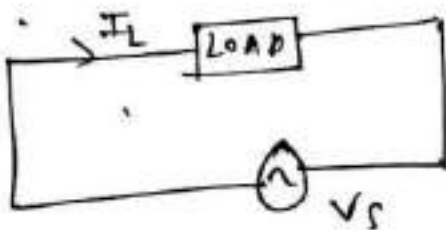- (i) Rating of generator's and Transformer's are proportional to their output current hence inversely proportional to power factor.
- (ii) The conducting material required is proportional to current so large conducting material required for transmission of power at low power factor.
- (iii) Copper loss is proportional to current so low power factor result high copper loss ($I^2 R$).


Power Factor Improvement → (i) by using capacitor with parallel to load ↓



- (ii) by using induction motor with phase advancer.

→ Ques. 18 A Series R-L-C Circuit consisting $R=20\Omega$, Inductance $0.2H$ and a capacitance of $150\mu F$ is connected across a $230V, 50Hz$ source. Calculate.
 (i) Impedance (ii) the current (iii) Power Factor (iv) Resonant frequency (v) quality factor.

Ans. →

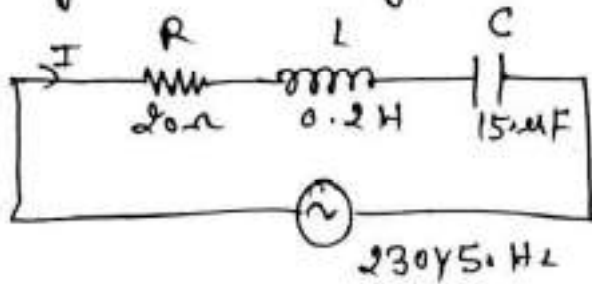

$$X_L = 2\pi fL$$

$$= 2 \times \pi \times 50 \times 0.2$$

$$= 62.83\Omega$$

$$X_C = \frac{1}{2\pi fC} = 21.22\Omega$$

(i) Impedance $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$= \sqrt{(20)^2 + (62.83 - 21.22)^2}$$

$$Z = 46.167\Omega$$


(ii) $I = \frac{V}{Z} = \frac{230}{46.167} = 4.98A$

(iii) $\cos\phi = \frac{R}{Z} = \frac{20}{46.167} = 0.4332$ lagging


(iv) $f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = 29.06Hz$. (v) $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

Ques. 19 Derive the Expression for band width in parallel R-L-C circuit. (Current Resonance)

Ans. →

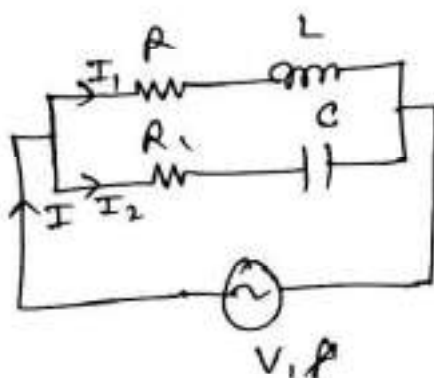

* Current is minimum at Resonance.

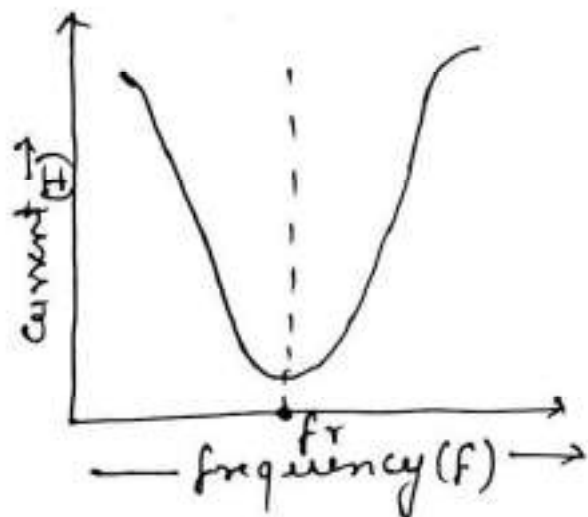

in case of Parallel circuit at bandwidth frequencies \therefore
 the net Susceptance B is equal to Conductance G So at
 frequency f_1 the Net Susceptance

$$B_{L1} - B_{C1} = G$$

at f_2 $B_{C2} - B_{L2} = G$

Then $Y = \sqrt{G^2 + B^2} = \sqrt{2G}$

and $\phi = \tan^{-1} B/G = \tan^{-1} 1 = 45^\circ$

Q Factor $Q = \frac{\text{Circulating Current } b/w L \& C}{\text{Line current}}$


now $I_C = 2\pi f_r C V$

$$I = V/L/CR = VCR/L$$

$$Q = \frac{I_C}{I} = \frac{2\pi f_r L}{R} \quad \text{but } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \text{neglecting } R \text{ in } f_r$$

Ques. 20

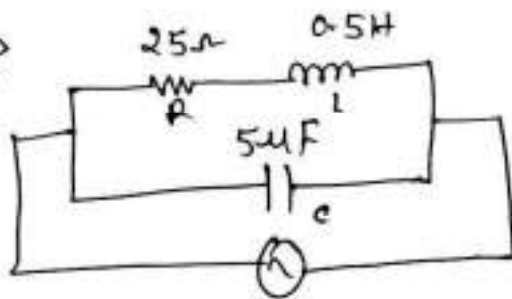

for the circuit find
 (i) Resonant frequency
 (ii) Impedance at Resonance
 (iii) Bandwidth
 (iv) Quality Factor

(i) $f_r = \frac{1}{2\pi\sqrt{LC - \frac{R^2}{L^2}}} = 100.34 \text{ Hz.}$

(ii) Impedance of ckt at Resonance $Z = L/CR = 4000 \Omega$

(iii) $\Delta f = R/2\pi L = \frac{25}{2\pi \times 0.5} = 7.958 \text{ Hz.}$

(iv) Quality Factor $Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{25} \sqrt{\frac{0.5}{5 \times 10^{-6}}} = 12.65$